



Digital Techniques 2

L4: Combinational Logic Design 2
(Logic Synthesis)



A Closer Look at the Logic Synthesis Process

mydesign.sv

```
always_comb
begin
  logic tmp;
  tmp = a[0];
  for (int i=1; i<=3; ++i)
    if (a[i] == '1')
      tmp = tmp ^ a[i];
  else
    break;
  Z = tmp;
end
```

```
set_max_delay 1 -to { Z }
```

mydesign.sdc

Constraints

RTL Code

RTL TRANSLATION


GENERIC LOGIC MODEL

(flip-flops and logic functions)

OPTIMIZATION &
MAPPING


Gate-Level Model
("netlist")

 Tip: Execute **File > Read** in Design Vision and select an RTL code file. Then create a schematic and you will see this intermediate form design.



mylib.db

 1. RTL code is translated into a generic logic model (ideal Boolean functions)
2. Designer sets constraints and selects a component library for a specific IC or FPGA technology
3. Synthesis tool optimizes logic and maps it to library components according to constraints






RTL Translation: Most Program Constructs Can Be Translated to Logic

Arithmetical/Logical Expressions

 
```
input logic [7:0] a, b,  
output logic [10:0] z);  
  
always_comb  
    z = a + (b << 2);
```



Many combinational implementations for arithmetic operations exist. More in next lecture.

Procedural Controls

 
```
if ( x == a )  
    z = sa;  
else if ( x == b )  
    z = sb;  
else if ( x == c )  
    z = sc;  
else  
    z = y;
```



if and case imply multiplexers.

Loops (finite)
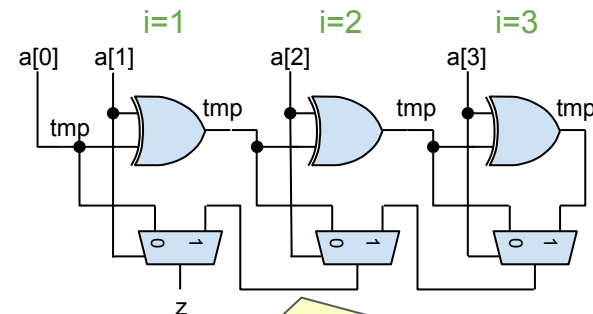
```
logic tmp;  
tmp = a[0];  
for (int i=1; i<=3; ++i)  
    if (a[i] == '1')  
        tmp = tmp ^ a[i];  
    else  
        break;  
Z = tmp;
```



Loops are unrolled which implies replication of logic.



Boolean Logic Optimization 1

Assume a design specified by the logic equations:

$$X = (A*B + A'*B')*(C + D) \quad // * = \text{AND}, + = \text{OR}, ' = \text{NOT}$$

$$Y = (A*B + A'*B')*(C'*D)$$

X and Y have a common term: $(A*B + A'*B')$


We can factor out the common term

$$K = (A*B + A'*B')$$

$$X = K*(C + D)$$

$$Y = K'*(C'*D)$$

 By implementing these **factored forms** of the functions fewer components are needed as logic in K is not replicated.






Boolean Logic Optimization 2

Using Boolean algebra, we can try to get rid of the parentheses to see where that might lead:

$$\begin{aligned} X &= (A*B + A'*B') * (C + D) \\ &= A*B*C + A'*B'*C + A*B*D + A'*B'*D \end{aligned}$$

$$\begin{aligned} Y &= (A*B)' * (A'*B')' * (C'*D) \\ &= (A' + B') * (A + B) * (C'*D) \\ &= (A'*A + A'*B + B'*A + B'*B) * (C'*D) \\ &= (A'*B + A*B') * (C'*D) \\ &= A'*B*C'*D + A*B'*C'*D \end{aligned}$$

 We get a **two-level** (AND-OR) implementation. The logic gate implementation looks different from the multi-level version, but the functions are logically equivalent to those on the previous slide.






Comparison of Factored and Two-Level Functions


FACTORED:

 - Longest delay path: 5 gates
- Complexity: 11 gates, 18 gate inputs (= ~36 transistors)
- Conclusion: Small but slow



TWO-LEVEL (S-O-P):

 - Longest delay path: 3 gates
- Complexity: 11 gates, 28 gate inputs
- Conclusion: Fast but big




(many other alternatives exist)





Technology Mapping

- After logic optimization, "reorganized" generic logic gates are replaced with real logic gates chosen from a component library
- The goal of this "mapping" is to cover the original "tree" with library cells so that some optimization goal is met
- Many kind of mapping optimizations are possible, e.g.
 - Selection of library gates to minimize delay or area
 - Power optimization by selecting high-drive gates ("X2") on critical paths and low-drive gates ("X1") and low-leakage gates on non-critical paths

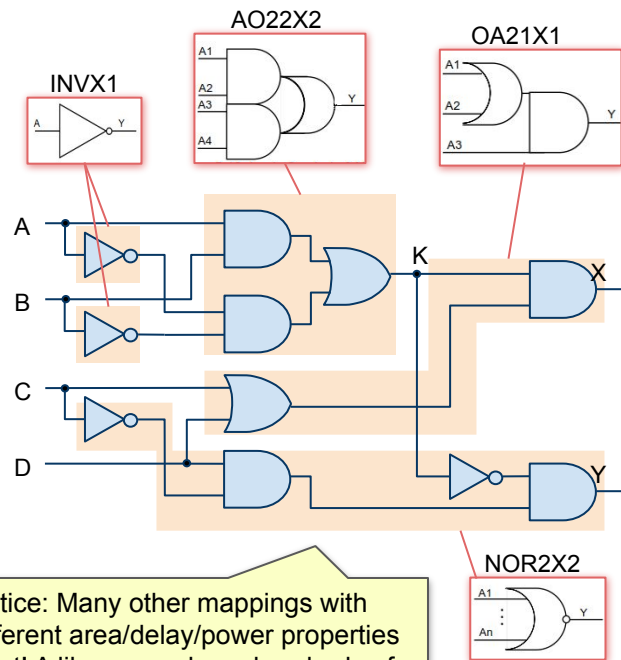


Notice: Many other mappings with different area/delay/power properties exist! A library can have hundreds of different gates.




Logic Libraries

- Components available in a target technology are described in a **logic library**
- Component models include:
 - Output pins' logic function
 - Area (corresponds to silicon area)
 - Power consumption
 - Timing
- Timing models are complex **nonlinear delay models** (NLDM) that specify output pins' rise and fall times as a function of input pins' transition times and output pins load capacitance values
- By changing the library, the design can be "mapped" to a different technology

INVX1_HVT

 

```
cell (INVX1_HVT) {  
  area : 1.27072 ;  
  cell_leakage_power : 6.832765e+03;  
  pin (Y) {  
    function : "(A)";  
    timing () {  
      related_pin : "A";  
      cell_rise ("del_1_7_7") {  
        index_1("0.016, 0.032, 0.064, 0.128, 0.256, 0.512, 1.024");  
        index_2("0.1, 0.25, 0.5, 1, 2, 4, 8");  
        values("0.0115926, 0.0124960, 0.0138466, 0.0162092, ... \\  
              "0.0152338, 0.0165709, 0.0185594, 0.0219617, ...", \  
internal_power () {  
  related_pin : "A";  
  rise_power ("power_outputs_1") {  
    index_1("0.016, 0.032, 0.064, 0.128, 0.256, 0.512, 1.024");  
    index_2("0.1, 0.25, 0.5, 1, 2, 4, 8");  
    values("0.9903715, 0.9937907, 0.9992987, 1.0122674, ... \  
          0.9807714, 0.9871708, 0.9850473, 0.9904108, ...", \  
}
```

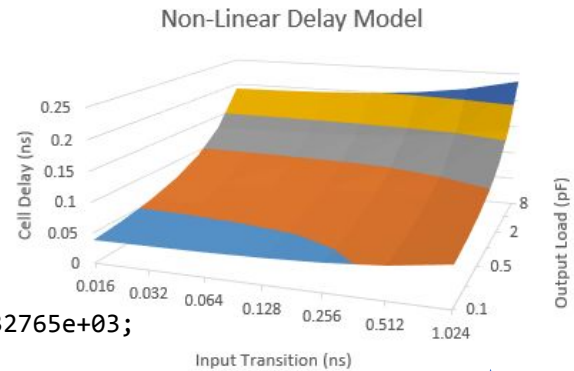




Logic Synthesis Usage

- For complex combinational logic functions with many inputs and outputs, a large number of different factorized forms exist
- To optimize a design, the designer sets a maximum delay constraint and lets the optimizer find a minimum-area (component count) solution the meets the constraint
- Minimal synthesis script (Synopsys Design Compiler)
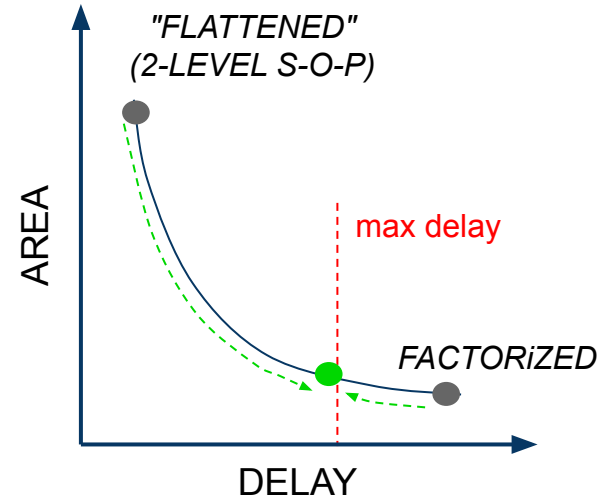
```
set target_library saed32hvt_tt1p05v25c.db  
read_file -format sverilog my_design.sv  
read_sdc my_constraints.sdc  
compile_ultra
```
- Learn more about logic synthesis in
521448S Physical Design of Digital Integrated Circuits



Area-delay trade-off of most combinational designs can be described as a "banana curve"