





Digital Techniques 2

L8: Sequential Logic 3



Finite-State Machine Controller Design

- FSM controllers are sequential circuits whose function is commonly defined as a **state chart** or table
- A state chart defines a circuit's output values and next state as a function of its inputs and current state
- This *abstraction* is well-suited for specification of control logic
- Example: Classic Nokia keyboard lock
 - Press key 1
 - Press key 2 within 1.5 seconds
- Control logic can be modeled as an FSM
- A counter can be used to measure time

 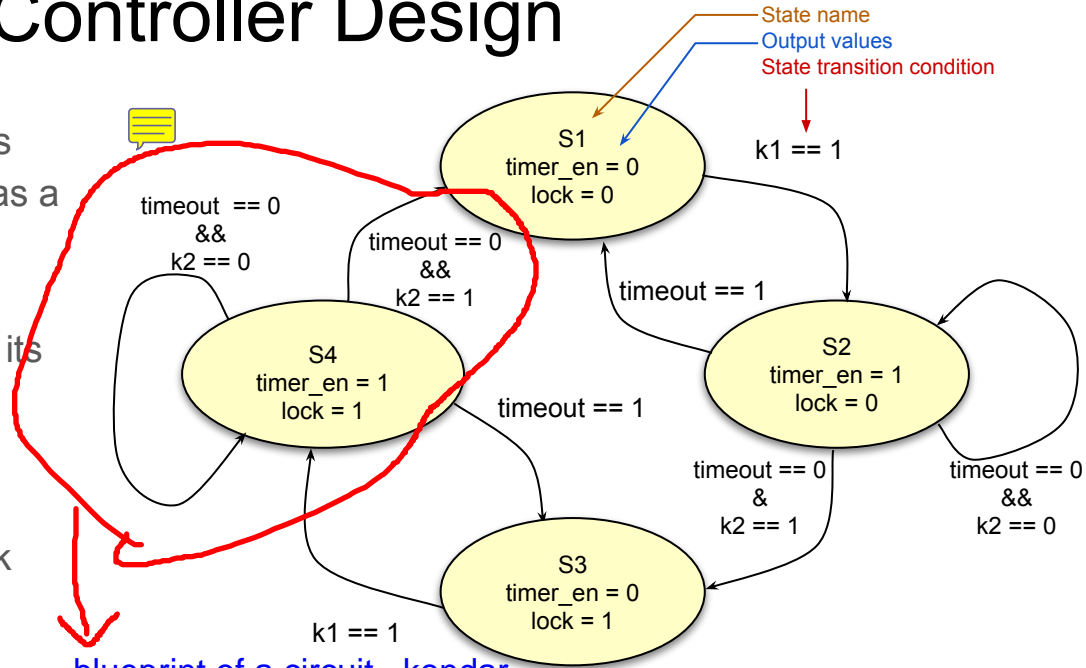



FSM Modeling for Synthesis: Two-Process Template


```
module fsm
  (input logic clk, rst_n, k1_in, k2_in, timeout_in,
   output logic lock_out, timer_en_out);

  enum logic [1:0] {S1 = 2'b00, S2 = 2'b01,
                   S3 = 2'b10, S4 = 2'b11 } state_r, next_state;
```

```
always_comb
begin : fsm_logic
  lock_out = '0; timer_en_out = '0; next_state = S1;
  case (state_r)
    S1:
      begin
        lock_out = '0;
        timer_en_out = '0;
        if (k1_in == '1)
          next_state = S2;
        else
          next_state = S1;
      end
    // Case items for other states...
  endcase
end : fsm_logic
```

See next slide for an explanation for this line.

 jodi kono current state change
hoi taile aida execute hbe



```
always_ff @(posedge clk or negedge rst_n)
begin : fsm_reg
  if (rst_n == '0)
    state_r <= S1;
  else
    state_r <= next_state;
end : fsm_reg
```

If you put the case statement here, you still need an *always_comb* with another case for the output decoder!

endmodule

ata current state ar value hold kore







About FSM Coding Styles

- There are advantages of using the two-process template: Many EDA tools recognize this coding style and can visualize the code as a state chart
- Coding style is the same for all FSMs, and the combinational part can be modelled using one **case** statement
- Use of **enumeration type** for state variable makes FSM debugging easier compared to use of binary codes
- **Assign default values** to FSM outputs in the beginning of the *always_comb* is a good way to avoid latches (FSM code can become very complicated)

FSM visualized in QuestaSim

  


Enumeration data types in simulation.




Modeling Moore- and Mealy-Type Outputs

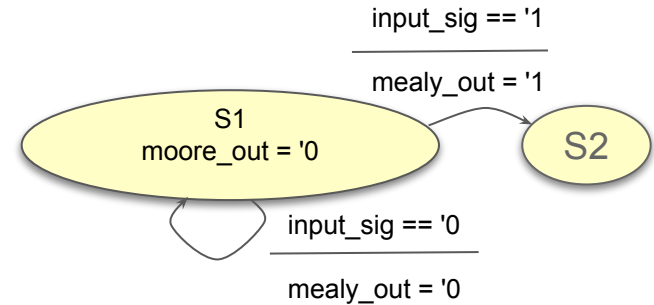- Mealy outputs depend on current state and inputs, while Moore outputs only depend on current state
- In practice, Mealy- and Moore-type behavior is usually combined in FSMs into one `always_comb`
- Mealy-type control is fast, but it can be risky



```
case (state_r)
  S1:
    begin
      moore_out= '0;
      if (input_sig == '1)
        begin
          next_state = S2;
          mealy_out = '1;
        end
      else
        begin
          next_state = S1;
          mealy_out = '0;
        end
      end
    end
end
```


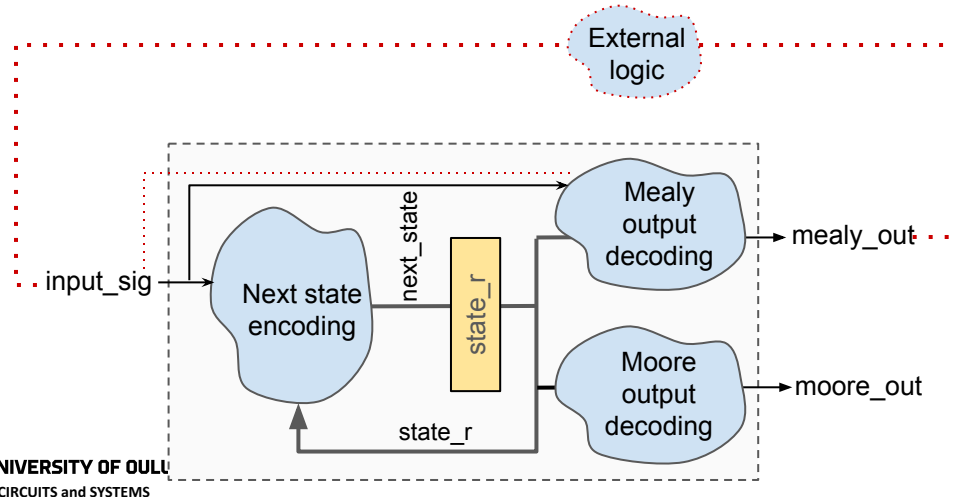
Combinational loop
can be accidentally
created when a
Mealy-controller is
connected to a
larger design.






Moore, Mealy and "Flag" Type Control

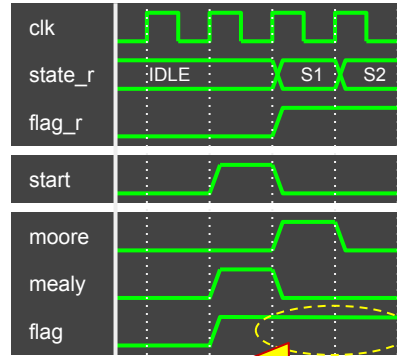 - In response to some event, Moore outputs have a one-cycle delay while Mealy outputs respond immediately
- Having a **flag** type output that "remembers" its state saves coding effort in controllers (you can define a new value only when it changes). It must be implemented with an additional flip-flop (flag_r)



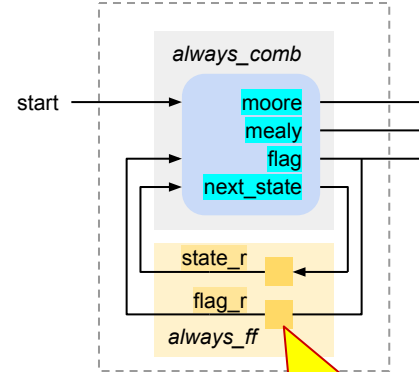flag toggled by **start**, stays on in **S1** and **S2** with no assignments in code.



An additional state bit must be allocated!

```
always_comb
begin
    moore = '0;
    mealy = '0;
    flag = flag_r;
    next_state = state_r;
    case (state_r)
        IDLE:
            if (start) begin
                flag = ~flag_r;
                mealy = '1;
                next_state = S1;
            end
        S1:
            begin
                moore = '1;
                next = S2;
            end
        S2:
            begin
                moore = '0;
                next = S3;
            end
    end
end
...
```



The Trouble with State Charts

- State charts are widely used in design, but they are often used in an *ad hoc* manner
- A specification should define the function unambiguously, but drawing a state chart that defines the function completely is tedious
- This leads to implicit assumptions about the function or input data to be made (example)
- In the example, the implicit assumptions could be either:


A) Input data is one-hot encoded

(only one of a,b,c is true at a time)

B) The priority order of inputs is a,b,c

- Mistakes can be made if RTL code is written by another person that does not know these assumptions

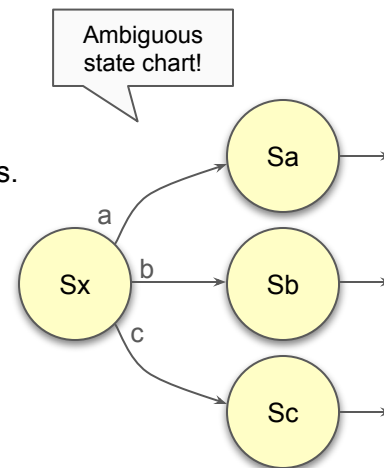Example: 3 inputs a,b,c
→ 8 possible combinations.
A *complete* chart would have 8 state transitions or complete transition condition functions (e.g. $a \cdot b' \cdot c'$)



A



?



B

```
case ({a,b,c})
  3'b100: next_state = Sa;
  3'b010: next_state = Sb;
  3'b001: next_state = Sc;
  default: next state = Sx;
endcase
```



```
if (a == '1)
  next_state = Sa;
else if (b == '1)
  next_state = Sb;
else if (c == '1)
  next_state = Sc;
else
  next_state = Sx;
```





Algorithmic State Machine (ASM) Descriptions

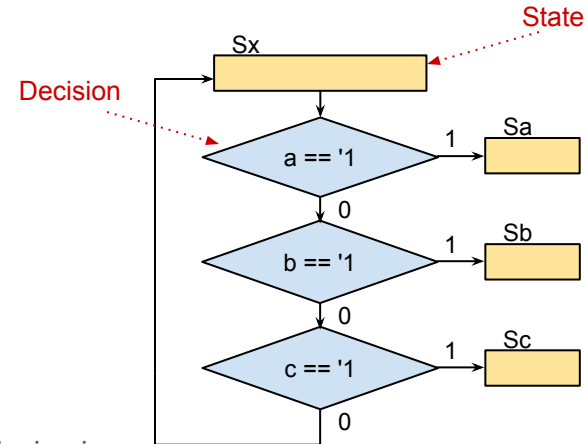 - Basic-form ASMs drawing rules:
 - Each state has only one output transition that goes to a two-way (yes-no) decision box or to another state
 - Decision boxes can be chained to form complex decision structures that can be coded with an **if - else if - ... - else** statement
- ASM forces the designer to consider all possible cases
- Moore and Mealy output definition:



RTL code design is easy: there is only one way the code an ASM chart!


```
case (state_r)
  Sx:
    if (a == '1)
      next_state = Sa;
    else if (b == '1)
      next_state = Sb;
    else if (c == '1)
      next_state = Sc;
    else
      next_state = Sx;
  Sa:
```





FSM State Encoding

- Assignment of state codes affects circuit complexity, performance and power consumption
- **Maximal encoding** minimizes number of flip-flops (e.g. binary code: 000, 001, 010)
- **One-hot** encoding yields simple combinational parts (e.g. 0001, 0010, 0100, 1000)
- **Gray-encoding** can minimize switching power caused by state changes ([example](#))
- Example on the right =>:
 - FSM with states s0, s1, s2, s3, s4
 - Output x *true* in state s1 and y *true* in state s2, s3, s4
 - Case A: Binary state encoding (000, 001, ...)
 - Case B: One-hot state encoding (00001, 00010, 00100, ...)
- You can define state encoding in code by assigning values to enum constants, or you can use synthesis tool settings

Case A)
Binary
encoding

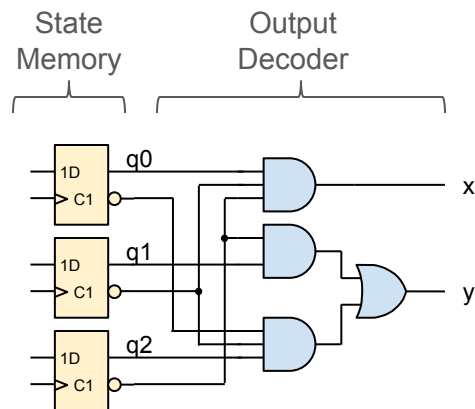 

Case B)
One-hot
encoding



One-hot encoding is favoured in FPGAs that often have an abundance of flip-flops.