



# Digital Techniques 2

## L5: Digital Arithmetic



# Fixed-Point Representation of Numbers

- Fixed-point (FXP) numbers have a fixed number of digits on the right hand side of the radix point. e.g.

$$0010_2 = 2_{10}$$

$$00.10_2 = 0.5_{10}$$

$$01.01_2 = 1.25_{10}$$

- The radix point is not represented in hardware, so you have to keep track of it!
- Signed FXP numbers are usually encoded in two's complement format



Two's complement encoding method:

- Select the number of bits in codewords (N)
- Encode numbers  $X \in [-2^{N-1}, 2^{N-1}-1]$  as  $2^N + X$  and **drop the N+1:th** bit, using codes [10..00, 10..01, ..., 01..11]
- Example: N = 4 bits,  
 $X = -1$   
 $X_{2's\ C} = 2^4 + (-1)$   
 $= 16 - 1 = 10000 - 0001 = 0\underline{1111}$
- We can now add positive and negative numbers:  
 $2 + (-1) = 0010 + 1111 = 1\underline{0001}$

To do: Check that this works for all positive and negative numbers. Study 2's complement number encoding until you understand how it works!



# Floating-Point Representation of Number

- Floating point number representation:  
**significant \* base<sup>exponent</sup>**
- In digital circuits, significant (S) and exponent (E) are (signed) fixed-point numbers, and base = 2
- FLP numbers are usually encoded by...
  - S = sign bit and unsigned value
  - Normalization: leading zeros in S value are omitted and E is adjusted accordingly
  - Exponent biasing: a constant value is added to exponent to make it positive (sign bit does not have to be stored)
- Floating point numbers have a (much) **larger dynamic range** [min, max] but **lower precision** than fixed point numbers
- In SystemVerilog the *float* type is **real**
- In general, floating point hardware is more complex than fixed-point
- Synthesis tools in general do not support floating point numbers, but that may be changing
- **In this course, we only use fixed-point numbers**



# Working with Fixed-Point Numbers

- You have to take care that radix points stay aligned in operations
- Example: Assume **A** has radix point at right end, and B at left end


```
logic [7:0] A, B;  
logic [15:0] C, tmp;  
A = 8'b00000001;  
B = 8'b10000000;
```

C = A + B; ☹️

tmp = A << 8;  
C = tmp + B 😊

**Tip:** It's a good idea to use "temp" variables to make sure sign and bit-length are handled correctly,

 
Let A = 00000001. ( $1_{10}$ ) and B = .10000000 ( $0.5_{10}$ )




 
# Manipulation of Signed FXP Numbers

- To obtain the **complement** of a 2's complement number, first invert all bits and then add a '1' to the inverted value:  
 $-111101 = 000010 + 1 = 000011 = 3$
- To make a signed FXP number longer, **sign extension** must be done:



- Shortening a number from left end:  
Value may be outside the new range, is often **saturated** (clipped to max possible value) before shortening.  
Example: Shorten 01111, 10001 and 00111 to four bits (to range  $[-8, 7]$ )  
 $01111 (15_{10}) \Rightarrow 0111 (7_{10})$   
 $10001 (-15_{10}) \Rightarrow 1000 (-8_{10})$   
 $00111 (7_{10}) \Rightarrow 0111 (7_{10})$
- Shortening from the right end:
  - Truncation** (just drop bits from the end)
  - Rounding** + truncation (better, but requires comparator hardware)



# Handling of Signed FXP Numbers in SystemVerilog Designs

- **logic** vector works like an unsigned binary number by default, but you can change the encoding if necessary:  
`logic [7:0] a;`  
`logic unsigned [7:0] b;`  
`logic signed [7:0] c;`
- SystemVerilog is a *weakly typed* language: operations on data items that are of incompatible types are allowed **according to language rules**
- Signedness handling is an area where you certainly have to know the rules

Assume a = 1110 (14)



```
module confused (input logic [3:0] a,  
                 output logic less_than_1,  
                 output logic less_than_minus_1);  
  
    always_comb  
    begin  
        if (a < 1) (14 < 1)  
            less_than_1= '1;  
        else  
            less_than_1= '0;  
  
        if (a < -1) (14 < 15)  
            less_than_minus_1= '1;  
        else  
            less_than_minus_1= '0;  
    end  
endmodule
```

SV Standard 11.4.4, "When one or both operands of a relational expression are unsigned, the expression shall be interpreted as a comparison between unsigned values."





# Some of SystemVerilog's Signedness Rules

- Decimal number literals (such as -1 or 4) are signed
- Based literal constants (**4'b1111**) are unsigned unless indicated with an 's' (**4'sb1111**)
- Packed logic arrays (**logic [3:0] x**) are unsigned unless declared *signed*
- Bit selects (**y[3]**) and range selects (**y[3:0]**) are always unsigned (gotcha!)
- Concatenation {y, x} result is unsigned
- Sign of an assignment depends only on operands ( $z = x + y$ ), not on left side
- An expression is signed only if all operands are signed

How to be sure? Use **\$signed** and **\$unsigned** conversion functions, e.g.

instead of **if (a < -1)** write **if (\$signed(a) < -1)** if a should be treated as signed

Survival guide: If you are uncertain, write a simple testbench program and try it out! (like in **labs/lab\_datatypes**)



# Some of SystemVerilog's Bit-Length Rules

- **int** and unspecified-length literals: 32 bits
- Operation **i op j** where **op** is **+**, **-**, **\***, **/**, **%**, **^** etc, ( $L(x)$  = length of  $x$ )  
 **$L(op) = \max(L(i), L(j))$**
- Operation **i op j**, where **op** is **<<**, **>>**, **\*\***, **<<<**, or **>>>**  
 **$L(op) = L(i)$**
- In assignments, right-hand side length also depends on left hand side length

```
logic [3:0] p, q;  
logic [3:0] r;  
p = 7;  
q = 9;
```

```
r = (p + q) >> 1; // r == 0
```

$L = \max(4, 4) \Rightarrow 7+9$  overflows

```
logic [3:0] p, q;  
logic [4:0] r;  
p = 7;  
q = 9;
```

```
r = (p + q) >> 1; // r == 8
```

$L(r) = 5 \Rightarrow$  no overflow

```
logic [3:0] p, q;  
logic [3:0] r;  
p = 7;  
q = 9;
```

```
r = (7 + q) >> 1; // r == 8
```

$L(7) = 32 \Rightarrow$  no overflow







# Arithmetic Hardware: Addition

- Binary addition works just like they taught you in school:


$A = 0110$ ,  $B = 1101$ ,  $A+B = 10011$

$$\begin{array}{r} 1100 \\ 0110 \\ + 1101 \\ \hline 10011 \end{array}$$



← Carry bits

- Number of bits in sum  $A + B$  is  **$\max(\text{bits in } A, \text{bits in } B) + 1$**
- To compute  $A - B$ , first form a 2's complement of  $B$ , then add


Building blocks:

 

Half adder

  


Full adder

 


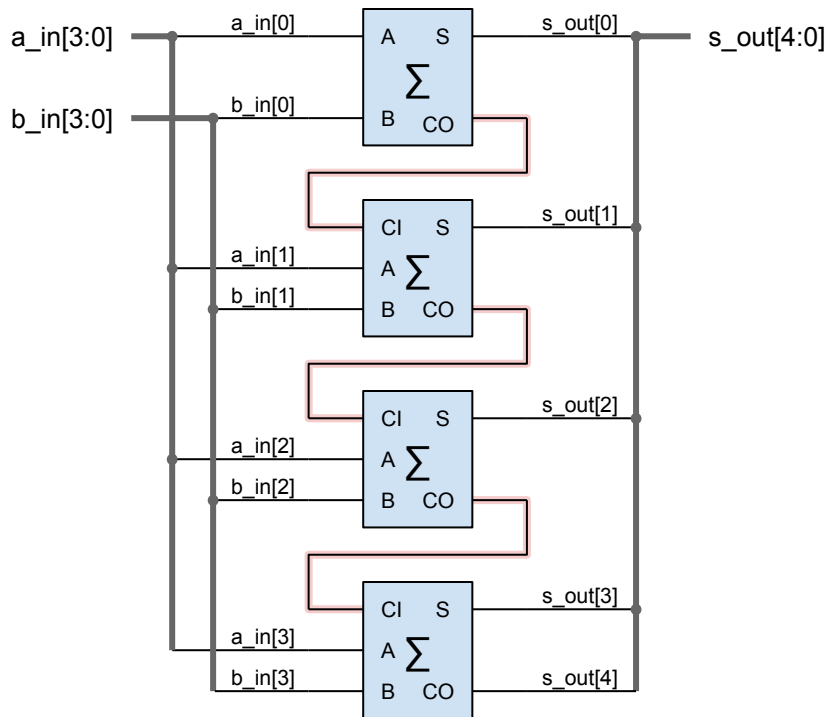
# Ripple-Carry Adder

- Simplest binary adder circuit
- 'Ripple' refers to the basic feature and limitation: the carry bit **ripples** from adder stage to the next
- Also known as a **carry-propagate adder** (see also: [adder/subtractor](#))
- Delay and complexity are proportional to the number of bits in the addends
- Speeding up carry propagation is the main objective in developing faster adder architectures (at the cost of additional hardware)



Area: 17 gates  
Delay: 7 gates



# Carry Look-Ahead Adder

$g[i]$  = Carry is generated from bits  $a\_in[i]$  and  $b\_in[i]$  if

$g[i] = a\_in[i] \cdot b\_in[i]$  (both are 1)

$p[i]$  = Bits  $a\_in[i]$  and  $b\_in[i]$  propagate a 'lower' carry if

$p[i] = a\_in[i] \oplus b\_in[i]$  (one is 1)

The  $i$ :th carry bit then has the logic function:

$$c[i] = g[i] + p[i] \cdot c[i-1]$$

Three first carry bits of an adder:


$$c[0] = g[0]$$

$$c[1] = g[1] + p[1] \cdot g[0]$$

$$c[2] = g[2] + p[2] \cdot g[1] + p[2] \cdot p[1] \cdot g[0]$$

Sum bit  $s\_out[i]$  is given by the XOR function:
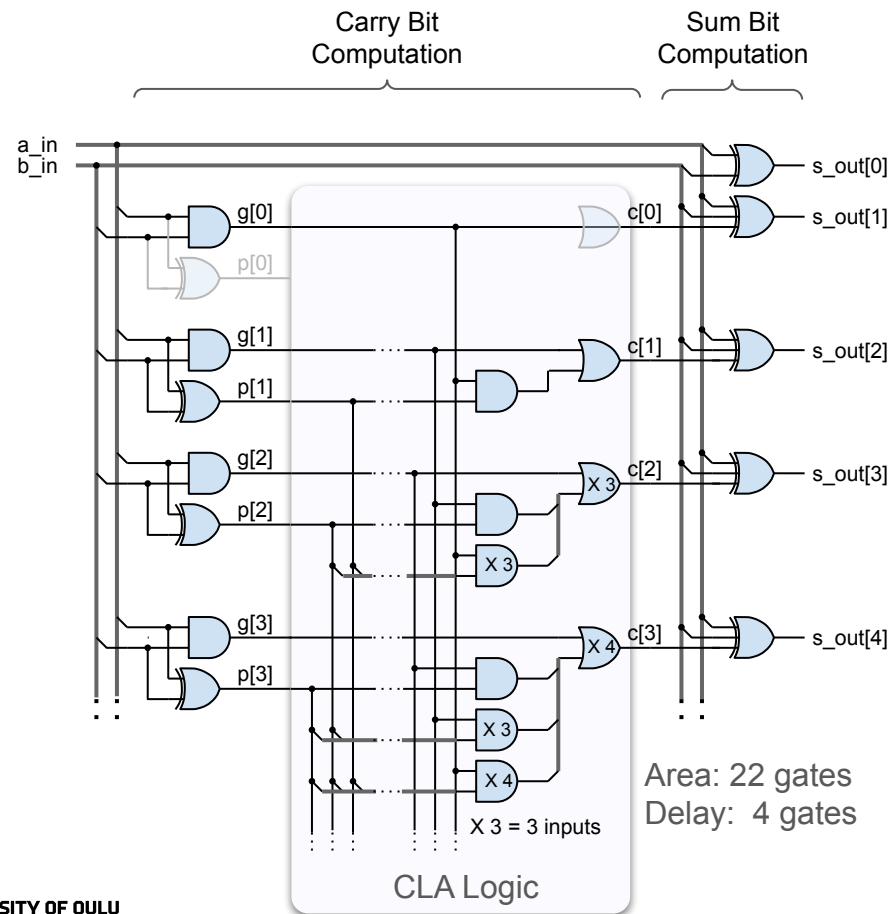
$$s\_out[i] = a\_in[i] \oplus b\_in[i] \oplus c[i-1]$$







# Carry-Save Addition

- Observation:  $A+B =$   
(Sum bits of  $A+B$ ) + (Carry bits of  $A + B$ )  $\ll 1$
- Sum and carry bits can be generated with **carry save adder** (CSA) that does not propagate carry
- **Final sum** is generated by adding sum bits with left-shifted carry bits in a carry propagate adder (CPA)
- To compute a **sum of many numbers**  $A+B+C+\dots$  we can delay the propagation of carry by creating intermediate sum and carry vectors in CSA:s and using a CPA as a last stage
- Optimal CSA tree is called a **Wallace tree**

CSA:

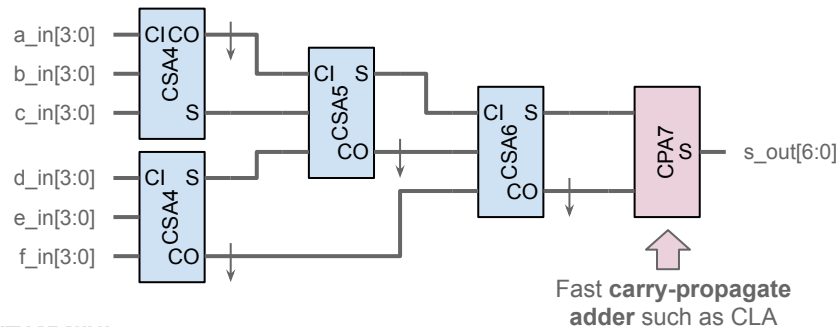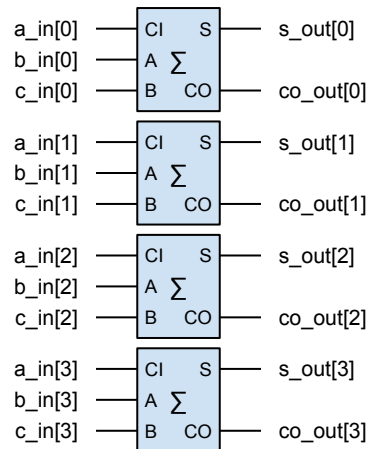



- Example:**  $5 \times 12 =$
- |  |   |  |  |       |   |   |   |      |
|--|---|--|--|-------|---|---|---|------|
|  |   |  |  |       |   |   |   | (12) |
|  |   |  |  | 1     | 1 | 0 | 0 |      |
|  | * |  |  | 0     | 1 | 0 | 1 | (5)  |
|  |   |  |  | <hr/> |   |   |   |      |
|  |   |  |  | 1     | 1 | 0 | 0 | P0   |
|  |   |  |  |       | 0 | 0 | 0 | P1   |
|  |   |  |  |       | 1 | 1 | 0 | P2   |
|  |   |  |  |       |   |   |   | P3   |
|  | + |  |  | 0     | 0 | 0 | 0 |      |
|  |   |  |  | <hr/> |   |   |   |      |
|  |   |  |  | 0     | 0 | 1 | 1 | 1    |
|  |   |  |  | 0     | 0 | 1 | 1 | 0    |
|  |   |  |  |       |   |   |   | 60   |

There are countless logic architectures for implementing arithmetic operations (+, -, \*, /, >, <, sin, cos, ...) in combinational or sequential logic, in bit-parallel and bit-serial format, with binary and 2's complement numbers etc. Consult the vast **computer arithmetic** literature to learn more.



# Fixed-Point Datapath Sizing Example

```
module fxp (input logic signed [8:0] c0, c1, c2,
            input logic signed [8:0] d0, d1, d2,
            output logic signed [8:0] r);
```

```
    logic signed [17:0] m0, m1, m2;
    logic signed [18:0] s0;
    logic signed [19:0] s1;
    logic signed [11:0] q;
```

```
    always_comb
    begin
```

```
        m0 = c0 * d0;
```

```
        m1 = c1 * d1;
```

```
        m2 = c2 * d2;
```

```
        s0 = m0 + m1;
```

```
        s1 = m2 + s0;
```

```
        q = s1 >>> 8; // drop fractional bits
```

```
        if (q > 9'sb01111111) // saturate to 9-bits
```

```
            r = 9'sb01111111;
```

```
        else if (q < 9'sb100000000)
```

```
            r = 9'sb100000000;
```


```
        else
```

```
            r = q;
```

```
    end
```

```
endmodule
```


Here we must know where the point is!

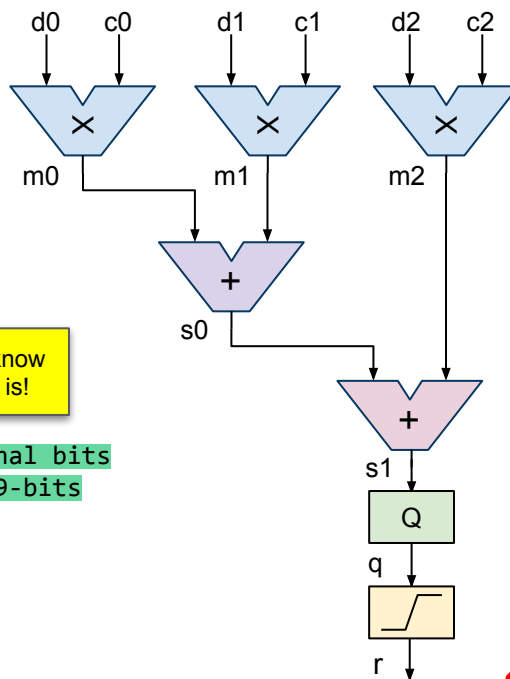

 **Input and output formats:**

d's and r: 9-bit signed integers

c's: 9 bit FXP numbers with the point after MSB. Decim range is [-1.0, 0.99609375]



duitar bit  
add holo

1 bit extra  
add holo

aida line tana

hoise jee point ar age

and pore kondar koi bit ase dekhari janno

Radix point position




UNIVERSITY OF OULU  
CIRCUITS and SYSTEMS



# Implementation of Arithmetic Operations in Synthesis

- Logic synthesis programs' RTL component libraries contain a selection of arithmetic components (+, -, \*, / etc)
- In *Design Compiler*, the RTL library is called *DesignWare*
- In RTL code translation, the synthesis program implements arithmetic operations detected in the code by inserting a library part in the unmapped design
- Library part implementation is automatically selected according to timing constraints in optimization
- Don't try to optimize the logic of an arithmetic part: it can make it slower (e.g. flattening to two-level will "optimize" CLA logic away!)

$S\_REG = A\_REG + B\_REG;$

 

RTL architecture generated from code.

RTL  
COMPONENT  
LIBRARY

CLA:  
delay=6  
area=11

RCA:  
delay=10  
area=5



# References

1. [IEEE Standard for SystemVerilog](#)  
11.6 Expression bit lengths  
11.8 Expression evaluation rules (signedness rules)
2. Harris (2007) Digital Design And Computer Architecture  
[Ch 5.2 - 5.3](#)